

VHDL

An introduction to modeling, analyzing, and simulating digital circuits

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG



- P. Ashenden: [The Designer's Guide to VHDL](#), Morgan Kaufmann Publishers, 1996.
- K. Chang: [Digital Design and Modeling with VHDL and Synthesis](#), IEEE Computer Society Press, 1997.
- S. Yalamanchili: [VHDL Starter's Guide](#), Prentice Hall, 1998.
- C.H. Roth: [Digital System Design using VHDL](#), PWS Publishing Company, 1998.

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

- VHDL
 - Very High Speed IC Hardware Description Language
- Main goal was developing a hardware description language to model digital circuits efficiently
 - Technology-independent
 - Various levels of abstraction
 - Behavioral, structural, or mixed descriptions
 - Structural hierarchy to model large systems
 - Modeling concurrent systems
 - Re-usability of specifications
 - Validation of designs based on the same description language for different levels of abstraction using a single simulation tool

- Started as an US Department of Defense project in 1983
- First IEEE standard was in 1987 (VHDL-87)
- Revised in 1993 (VHDL-93)
- Development still in progress (VHDL-2000/2002/2008)
- Nowadays, ...
 - VHDL is the standard for most of the US and EU industry
 - Mainly used for hardware generation (not all VHDL statements are synthesizable!)

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

Typically, VHDL is used for the following tasks

- 1 Modeling the behavior of a digital system
- 2 Validating the developed design
- 3 Translating the digital system into real hardware (using appropriate synthesis tools)
 - ASICs – Application-Specific Integrated Circuits
 - FPGAs – Field Programmable Gate Arrays



ASICs – Application-Specific Integrated Circuits

- Customized for a particular use
- Functionality cannot be changed after manufacturing

FPGAs – Field Programmable Gate Arrays

- Designed to be configured by the customers after manufacturing
- Programmable logic elements & interconnects (sometimes even embedded microprocessors)
- Can be reconfigured indefinitely often (i.e. to fix bugs)
- May be cheaper than ASICs (smaller designs / lower production volumes)
- Usually, slower and less power efficient than real hardware

ASICs – Application-Specific Integrated Circuits

- Customized for a particular use
- Functionality cannot be changed after manufacturing

FPGAs – Field Programmable Gate Arrays



- Designed to be configured by the customers after manufacturing
- Programmable logic elements & interconnects (sometimes even embedded microprocessors)
- Can be reconfigured indefinitely often ⇒ prototyping
- May be cheaper than ASICs (smaller designs / lower production volumes)
- Usually, slower and less power efficient than real hardware

FPGAs – Field Programmable Gate Arrays

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

  


Which one is the FPGA?

FPGAs – Field Programmable Gate Arrays


Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

 



Xilinx Virtex FPGA

 

AMD Phenom CPU

FPGAs – Field Programmable Gate Arrays

Albert-Ludwigs-Universität Freiburg

  


FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

 


FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

 


FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

 

Altera Cyclone II FPGA


- About 240,000 bits of RAM
- About 18,000 logic blocks
- Supports softcore processors

FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg




UNI
FREIBURG

 

Power supply

FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg

 


USB & JTAG interface

FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

 


50 MHz quartz

FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

 


512 kB SRAM, 8 MB SDRAM

FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

 


Push buttons, LEDs, display

FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

 

General purpose I/O pins

FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG




Servo control pins

FPGA Boards used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

 

Audio chip


Altera Software used in Freiburg

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

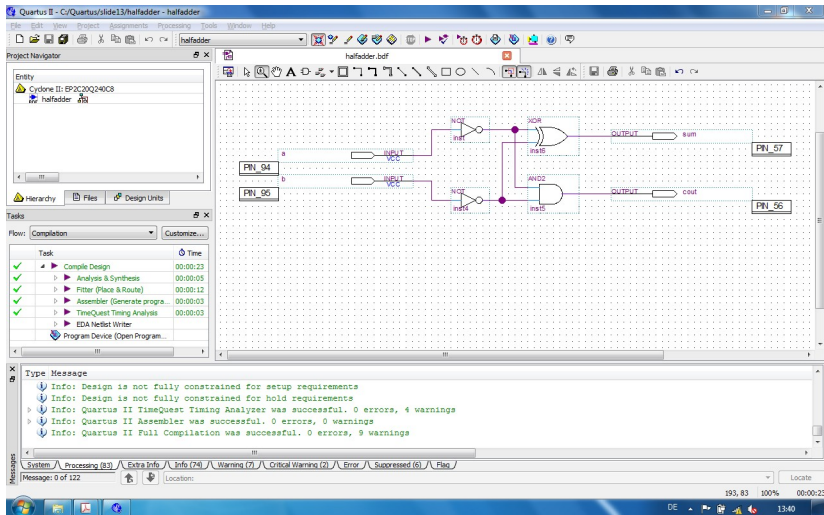- Quartus II Web Edition Version 10.1
- Modelsim Altera Starter Edition Version 6.6d
- Nios II Embedded Design Suite Version 10.1



The screenshot displays the Quartus II Web Edition interface. The main workspace shows a logic diagram for a circuit named 'halfadder.bdf'. The circuit has two inputs, 'a' (PIN 04) and 'b' (PIN 06), each connected to an 'INPUT' block. The outputs are 'sum' (PIN 57) and 'cout' (PIN 56). The logic consists of two XOR gates (labeled 'XOR') and two AND gates (labeled 'AND2'). The XOR gates take 'a' and 'b' as inputs, and their outputs are connected to the 'sum' output. The AND gates take 'a' and 'b' as inputs, and their outputs are connected to the 'cout' output.

The left sidebar contains the Project Navigator, showing the project hierarchy with 'Cyclone II: EP2K10K10C8' and 'halfadder'. Below it is the Tasks window, which shows a list of tasks and their completion times:

Task	Time
Compile Design	00:00:23
Analysis & Synthesis	00:00:05
Fitter (Place & Route)	00:00:12
Assembler (Generate program)	00:00:03
TimeQuest Timing Analyzer	00:00:03
EDA Netlist Writer	
Program Device (Open Program)	

At the bottom, the Type Message window shows the following messages:

- Info: Design is not fully constrained for setup requirements
- Info: Design is not fully constrained for hold requirements
- Info: Quartus II TimeQuest Timing Analyzer was successful. 0 errors, 4 warnings
- Info: Quartus II Assembler was successful. 0 errors, 0 warnings
- Info: Quartus II Full Compilation was successful. 0 errors, 9 warnings


The status bar at the bottom indicates 'Message: 0 of 122' and 'Location:'. The system tray shows the date and time as '13:40'.

Modelsim Altera Starter Edition

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

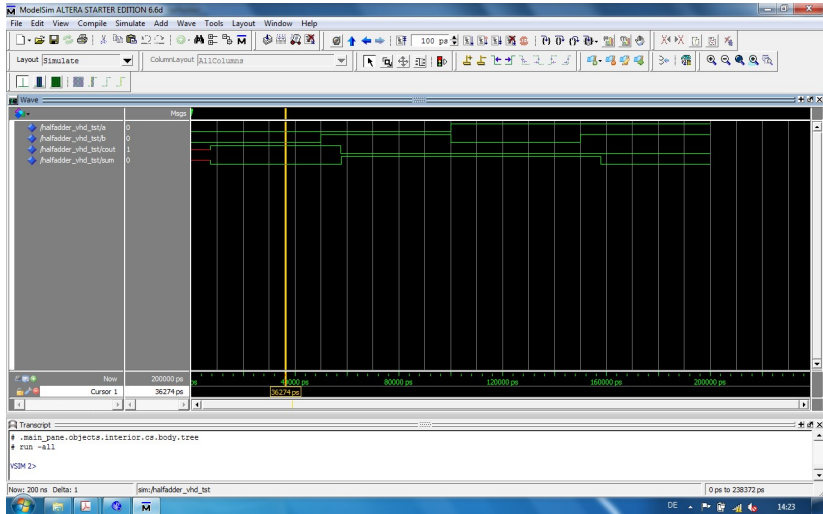

Nios II Embedded Design Suite

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

The screenshot displays the Nios II IDE interface. The main window shows a C program named `servo.c` with the following code:

```
int main()
{
    int command = 0;
    int d = 0;

    IOWR(SERVO_0, 0, 0);
    IOWR(SERVO_1, 0, 0);

    while (command == 0)
    { command = IORD_S2DIRECT(KEYS, 0) ^ 0xF; }

    while (1)
    {
        for (d = 0; d < 4; d++)
        {
            IOWR(SERVO_0, 0, 507);
            IOWR(SERVO_1, 0, 665);
            wait(1300);

            IOWR(SERVO_0, 0, 665);
            IOWR(SERVO_1, 0, 665);
            wait(610);
        }
    }
}
```

The console window at the bottom shows the compilation output:

```
C:\Build\servo
Linking %servo.eif...
Info: (servo.eif) 21 KBytes program size (code + initialized data).
Info:          11 KBytes free for stack + heap.
Post-processing to create onchip_sram.hex
Hardware simulation is not enabled for the target SOPC Builder system. Skipping creation of hardware simulation model
contents and simulation symbol files. (Note: This does not affect the instruction set simulator.)
Build completed in 17.472 seconds
```

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 **First examples**
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation


Examples – OR Gate

Albert-Ludwigs-Universität Freiburg



Entity
 
```
entity orGate is  
  port ( a, b: in bit; c: out bit );  
end orGate;
```



Entity

```
entity orGate is  
  port ( a, b: in bit; c: out bit );  
end orGate;
```

Entities

- Define the interface
- Entity name = file name
- Ports
 - Inputs ⇒ **in**
 - Outputs ⇒ **out**
 - Bi-directional ⇒ **inout**
 - ...
- Remarks
 - Outputs cannot be read
 - Inputs cannot be written to

Examples – OR Gate

Albert-Ludwigs-Universität Freiburg



Entity

```
entity orGate is  
  port ( a, b: in bit; c: out bit );  
end orGate;
```

Architecture(s)

```
architecture arch1 of orGate is  
begin  
  c <= a or b;  
end arch1;
```

```
architecture arch2 of orGate is  
begin  
  c <= '1' when (a = '1' or b = '1') else '0';  
end arch2;
```

Architectures define the implementation of an entity

Examples – Full Adder

Albert-Ludwigs-Universität Freiburg



Entity

```
entity fullAdder is  
  port ( a, b, cin: in bit; sum, cout: out bit );  
end fullAdder;
```



Examples – Full Adder (Behavioral Description)

Albert-Ludwigs-Universität Freiburg



Entity

```
entity fullAdder is  
  port ( a, b, cin: in bit; sum, cout: out bit );  
end fullAdder;
```

Architecture

```
architecture behavior of fullAdder is  
  begin  
    sum <= (a xor b) xor cin;  
    cout <= (a and b) or (a and cin) or (b and cin);  
  end behavior;
```


Examples – Full Adder (Structural Description)

Albert-Ludwigs-Universität Freiburg



Entity
 
```
entity fullAdder is  
  port ( a, b, cin: in bit;  
         sum, cout: out bit );  
end fullAdder;
```



Architecture

```
architecture structure of fullAdder is  
  component halfAdder port ( a, b: in bit; sum, cout: out bit ); end component;  
  component orGate port ( a, b: in bit; c: out bit ); end component;  
  signal x, y, z: bit;  
begin  
  i1: halfAdder port map ( a, b, x, y );  
  i2: halfAdder port map ( x, cin, sum, z );  
  o1: orGate port map ( y, z, cout );  
end structure;
```

Examples – Full Adder (Structural Description)

Albert-Ludwigs-Universität Freiburg



halfAdder

```
entity halfAdder is  
  port ( a, b: in bit; sum, cout: out bit );  
end halfAdder;
```

```
architecture behavior of halfAdder is  
begin  
  sum <= a xor b;  
  cout <= a and b;  
end behavior;
```

orGate

```
entity orGate is  
  port ( a, b: in bit; c: out bit );  
end orGate;
```

```
architecture behavior of orGate is  
begin  
  c <= '1' when (a = '1' or b = '1') else '0';  
end behavior;
```

Entity & Architecture

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity counter is
  port (
    clk: in std_logic;
    q1, q2: out std_logic_vector (4 downto 0) );
end counter;

architecture behavior of counter is
  signal cnt: std_logic_vector (4 downto 0) := "00000";
begin
  process ( clk )
  begin
    if clk = '1' then cnt <= cnt + 1; end if;
    q1 <= cnt;
  end process;
  q2 <= cnt;
end behavior;
```

Processes

- Are declared within an architecture and are concurrent statements
 - But, all statements inside a process are executed sequentially!
 - Signal updates within a process are not done immediately!
 - Processes will be executed whenever there is an event on one of the signals of the corresponding “sensitivity list”
- ⇒ In our example, the process counts the number of rising edges that occur on signal clk

Examples – Counter (using signals)

Albert-Ludwigs-Universität Freiburg



Entity & Architecture

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity counter is
  port (
    clk: in std_logic;
    q1, q2: out std_logic_vector (4 downto 0) );
end counter;

architecture behavior of counter is
  signal cnt: std_logic_vector (4 downto 0) := "00000";
begin
  process ( clk )
  begin
    if clk = '1' then cnt <= cnt + 1; end if;
    q1 <= cnt;
  end process;
  q2 <= cnt;
end behavior;
```

Values provided by std_logic

- '0' – logical zero
- '1' – logical one
- 'U' – uninitialized
- 'X' – unknown
- 'Z' – high impedance
- 'W' – weak unknown
- 'L' – weak low
- 'H' – weak high
- '-' – don't care

Examples – Counter (using variables)

Albert-Ludwigs-Universität Freiburg



Entity & Architecture

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity counter is
  port (
    clk: in std_logic;
    q: out std_logic_vector (4 downto 0) );
end counter;

architecture behavior of counter is
begin
  process ( clk )
    variable cnt: std_logic_vector (4 downto 0) := "00000";
  begin
    if clk = '1' then cnt := cnt + 1; end if;
    q <= cnt;
  end process;
end behavior;
```

Variables

- Appear in processes only
- Initial values can be set for simulation purpose
- Variables are updated without any time delay!


- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation


There are several methods to validate hardware components


- Formal verification techniques
 - Equivalence checking
 - Symbolic model checking
 - Bounded model checking
- Simulation (complete vs. incomplete)


Here, the focus is on simulating VHDL designs using testbenches (by means of some examples)


Testbench

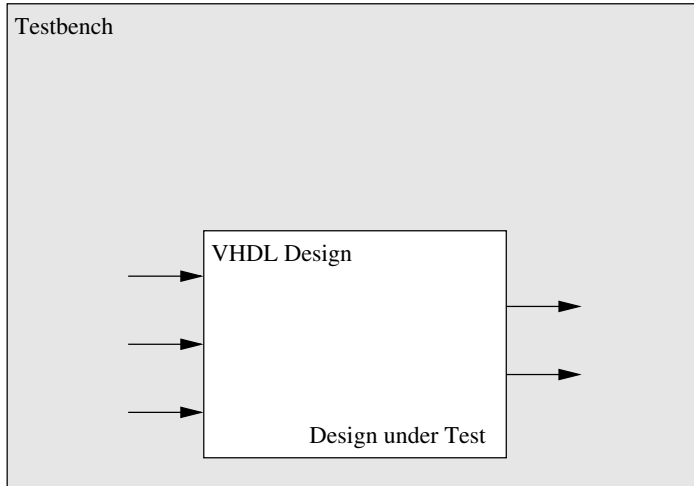

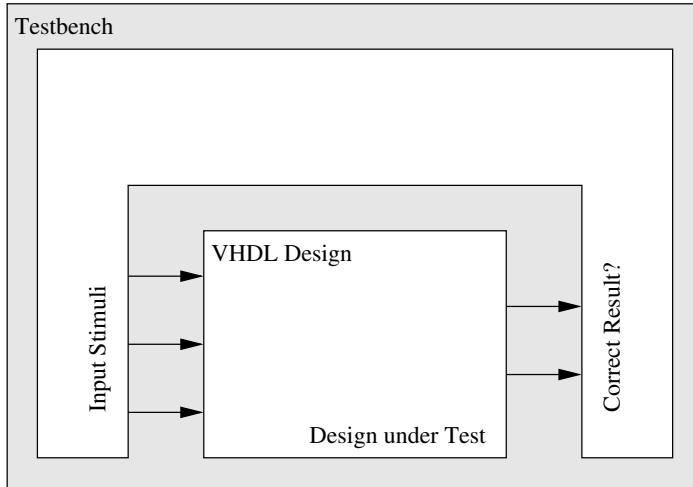

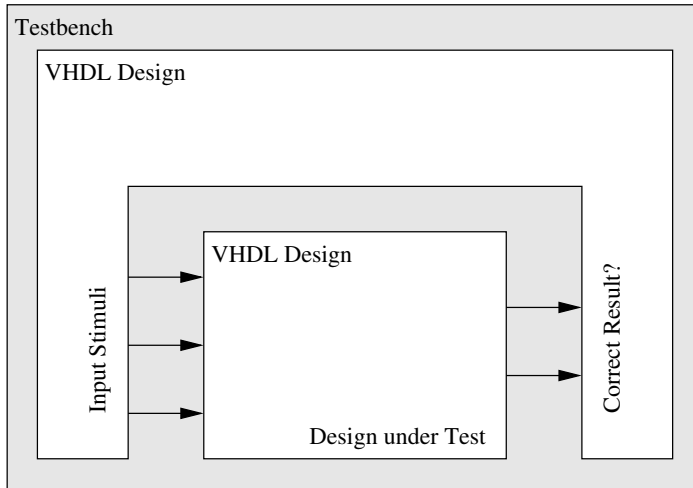

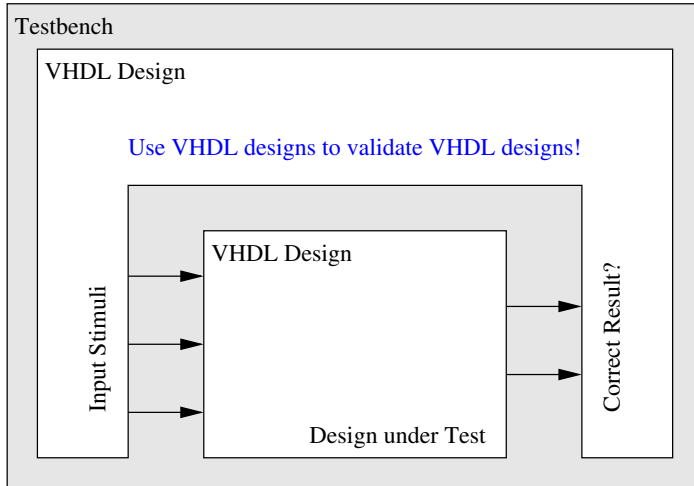

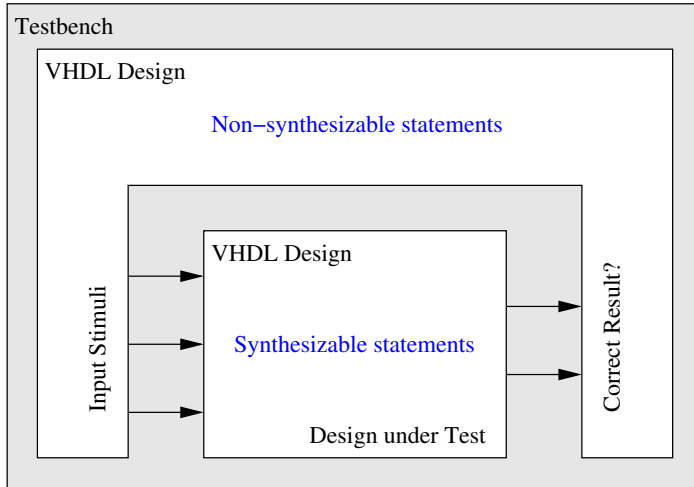

Testbenches – OR Gate (Slide 19)

Albert-Ludwigs-Universität Freiburg



Testbench orGate

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity orGate_vhd_tst is  
end orGate_vhd_tst;  
  
architecture orGate_arch of orGate_vhd_tst is  
  signal a, b, c : std_logic;  
  component orGate  
    port ( a, b : in std_logic; c : out std_logic );  
  end component;  
begin  
  i1 : orGate port map ( a, b, c );  
  process  
    begin  
      a <= '0'; b <= '0'; wait for 50 ns;  
      a <= '0'; b <= '1'; wait for 50 ns;  
      a <= '1'; b <= '0'; wait for 50 ns;  
      a <= '1'; b <= '1'; wait for 50 ns;  
      wait;  
    end process;  
end orGate_arch;
```

Testbenches – Full Adder (Slides 21–23)

Albert-Ludwigs-Universität Freiburg



Testbench fullAdder

```
library ieee;
use ieee.std_logic_1164.all;

entity fullAdder_vhd_tst is
end fullAdder_vhd_tst;

architecture fullAdder_arch of fullAdder_vhd_tst is
    signal a, b, cin, sum, cout : std_logic;
    component fullAdder
        port ( a, b, cin : in std_logic; sum, cout : out std_logic );
    end component;
begin
    i1 : fullAdder port map ( a, b, cin, sum, cout );
    process
    begin
        a <= '0'; b <= '0'; cin <= '0'; wait for 50 ns;
        a <= '0'; b <= '0'; cin <= '1'; wait for 50 ns;
        -- more test cases...
        a <= '1'; b <= '1'; cin <= '1'; wait for 50 ns;
        wait;
    end process;
end fullAdder_arch;
```

Testbenches – Counter (Slide 24)

Albert-Ludwigs-Universität Freiburg



Testbench counter

```
library ieee;
use ieee.std_logic_1164.all;

entity counter_vhd_tst is
end counter_vhd_tst;

architecture counter_arch of counter_vhd_tst is
    signal clk : std_logic;
    signal q1, q2 : std_logic_vector (4 downto 0);
    component counter
        port ( clk : in std_logic; q1, q2 : out std_logic_vector (4 downto 0) );
    end component;
begin
    i1 : counter port map ( clk, q1, q2 );
    process
    begin
        clk <= '0'; wait for 50 ns;
        clk <= '1'; wait for 50 ns;
        clk <= '0'; wait for 50 ns;
        -- more test cases...
    wait;
    end process;
end counter_arch;
```

Testbenches – Counter (Slide 24)

Albert-Ludwigs-Universität Freiburg




Altera provides two modes of simulation

- RTL: simulates the design without timing information
- Gate-Level: simulates the design with post-fit timing information (i.e. taking FPGA-specific gate delays into account, more realistic model)

Testbenches – Counter (Slide 24, RTL)

Albert-Ludwigs-Universität Freiburg

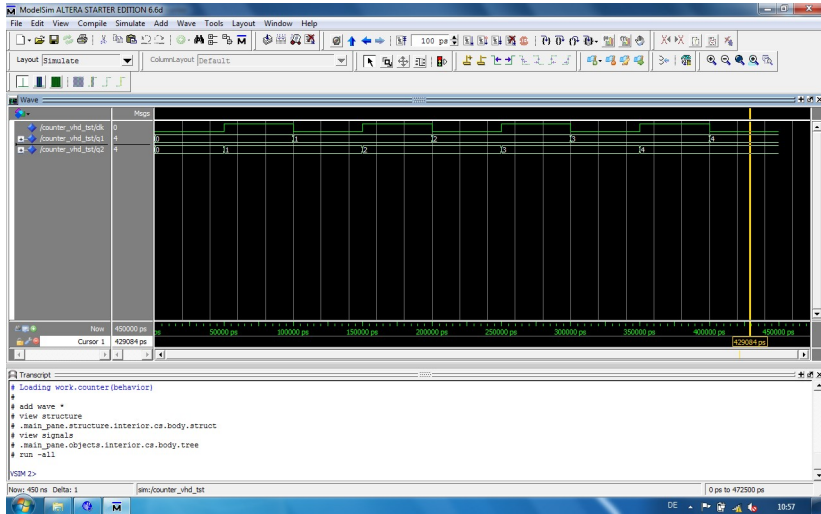

Testbenches – Counter (Slide 24, Gate-Level)

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

The screenshot displays the ModelSim ALTERA STARTER EDITION 6.6d interface. The main window shows a simulation wave with three signals: /counter_vhd_tstclk (0), /counter_vhd_tstq1 (x), and /counter_vhd_tstq2 (x). The wave shows a clock signal (green) and two data signals (red) that are high during the clock pulses. The time scale is 100 ps. The transcript window shows the following commands:

```
Time: 0 ps Iteration: 0 Region: /counter_vhd_tst File: C:/Quartus/slide24/simulation/modelsim/counter.vht
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run -all
VSM: 2>
```

The status bar at the bottom indicates the current time is 450 ns, the delta is 1, and the simulation is running at 0 ps to 472500 ps.

Entity & Architecture

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity counter is
  port ( clk: in std_logic; q1, q2: out std_logic_vector (4 downto 0) );
end counter;

architecture behavior of counter is
  signal cnt: std_logic_vector (4 downto 0) := "00000";
begin
  process ( clk )
  begin
    if clk = '1' then cnt <= cnt + 1; end if;
    q1 <= cnt;
  end process;
  q2 <= cnt after 25 ns;
end behavior;
```

Testbench counter

```
library ieee;
use ieee.std_logic_1164.all;

entity counter_vhd_tst is
end counter_vhd_tst;


architecture counter_arch of counter_vhd_tst is
  signal clk : std_logic;
  signal q1, q2 : std_logic_vector (4 downto 0);
  component counter
    port ( clk : in std_logic; q1, q2 : out std_logic_vector (4 downto 0) );
  end component;
begin
  i1 : counter port map ( clk, q1, q2 );
  process
  begin
    clk <= '0'; wait for 50 ns;
    clk <= '1'; wait for 50 ns;
    clk <= '0'; wait for 50 ns;
    -- more test cases...
  wait;
  end process;
end counter_arch;
```

Testbenches – Modified Counter (RTL)

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

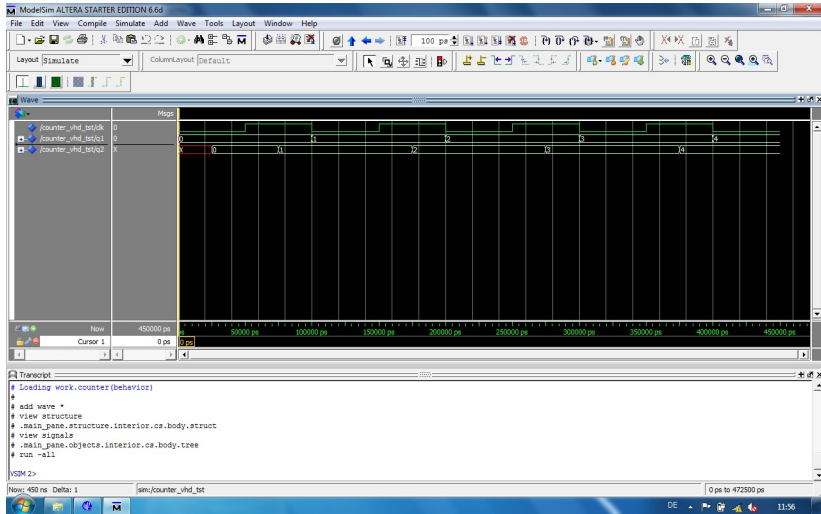

Testbenches – Modified Counter (Gate-Level)

Albert-Ludwigs-Universität Freiburg



The screenshot displays the ModelSim ALTERA STARTER EDITION 6.6d interface. The main window shows a simulation wave with three signals: `/counter_vhd_tstclk`, `/counter_vhd_tstq1`, and `/counter_vhd_tstq2`. The wave shows a clock signal and two data signals. The transcript window at the bottom shows the following commands:

```
Transcript
# Time: 0 ps Iteration: 0 Region: /counter_vhd_tst File: C:/Quartus/slide35/simulation/modelsim/counter.vht
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run -all
VSBM 2>
```

The status bar at the bottom indicates the current time is 450 ns, the delta is 1 ps, and the simulation is running from 0 ps to 472500 ps.

Testbenches – Counter (Slide 25)

Albert-Ludwigs-Universität Freiburg



Testbench counter

```
library ieee;
use ieee.std_logic_1164.all;

entity counter_vhd_tst is
end counter_vhd_tst;

architecture counter_arch of counter_vhd_tst is
  signal clk : std_logic;
  signal q : std_logic_vector (4 downto 0);
  component counter
    port ( clk : in std_logic; q : out std_logic_vector (4 downto 0) );
  end component;
begin
  i1 : counter port map ( clk, q );
  process
  begin
    clk <= '0'; wait for 50 ns;
    clk <= '1'; wait for 50 ns;
    clk <= '0'; wait for 50 ns;
    -- more test cases...
  wait;
  end process;
end counter_arch;
```

Testbenches – Half Adder (Slide 13)

Albert-Ludwigs-Universität Freiburg



Testbench halfAdder

```
library ieee;
use ieee.std_logic_1164.all;

entity halfadder_vhd_tst is
end halfadder_vhd_tst;

architecture halfadder_arch of halfadder_vhd_tst is
  signal a, b, cout, sum : std_logic;
  component halfadder
    port ( a, b : in std_logic; cout, sum : out std_logic );
  end component;
begin
  i1 : halfadder port map ( a, b, cout, sum );
  process
  begin
    report "Validating...";
    a <= '1'; b <= '0'; wait for 50 ns;
    assert (cout = '0' and sum = '1') report "Error";
    -- more test cases...
    report "Done...";
    wait;
  end process;
end halfadder_arch;
```

Testbenches – Half Adder (Slide 13)

Albert-Ludwigs-Universität Freiburg



ModelSim ALTERA STARTER EDITION 6.6d

File Edit View Compile Simulate Add Wave Tools Layout Window Help

Layout Simulate ColumnLayout Default

Wave

Msgs

1 /halfadder_vhd_tst/a
1 /halfadder_vhd_tst/b
0 /halfadder_vhd_tst/c
0 /halfadder_vhd_tst/d

Now: 200000 ps
Cursor 1: 0 ps

40000 ps 80000 ps 120000 ps 160000 ps 200000 ps

Transcript

```
Time: 0 ps Iteration: 0 Region: /halfadder_vhd_tst File: C:/Quartus/slide13/simulation/modelsim/halfadder.vht
* add wave *
* view structure
* main_gate_structure.interior.cs.body_struct
* view signals
* run -all
** Note: Validating...
Time: 0 ps Iteration: 0 Instance: /halfadder_vhd_tst
** Note: Done...
Time: 200 ns Iteration: 0 Instance: /halfadder_vhd_tst
```

Now: 200 ns Delta: 1 smc:/halfadder_vhd_tst 0 ps to 210 ns

DE 11:20

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

Identifiers

- Allowed characters: 'a' to 'z', '0' to '9', and '_'
- Must begin with a letter and the last one cannot be an underscore
- Only one underscore allowed at a time
- Case insensitive ('myBus' and 'mybus' refer to the same VHDL object)
- Reserved words cannot be used
- Examples
 - Allowed identifiers: myBus, my_bus_8_bit
 - Illegal identifiers: _bus, 8Bit_bus, myBus__8Bit

Reserved words in VHDL-93

abs, access, after, alias, all, and, architecture, array, assert, attribute, begin, block, body, buffer, bus, case, component, configuration, constant, disconnect, downto, else, elsif, end, entity, exit, file, for, function, generate, generic, group, guarded, if, impure, in, inertial, inout, is, label, library, linkage, literal, loop, map, mod, nand, new, next, nor, not, null, of, on, open, or, others, out, package, port, postponed, procedure, process, pure, range, record, register, reject, rem, report, return, rol, ror, select, severity, signal, shared, sla, sll, sra, srl, subtype, then, to, transport, type, unaffected, units, until, use, variable, wait, when, while, with, xnor, xor



Comments

- Comments start with `--`
- Example
 - `a <= '1'; -- Signal 'a' is set to logical 1.`

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

Standard data types

- bit: 0, 1
- boolean: true, false
- character: most ASCII characters
- integer: $-(2^{31} - 1), \dots, (2^{31} - 1)$
- real: $-1.7e38, \dots, 1.7e38$
- time: 1 fs, ..., 1 hr

User-defined integer and floating-point data types

- Syntax
 - **type** identifier **is** type_definition;
 - **subtype** sub_identifier **is** identifier [type_definition];
- Examples
 - **type** small **is range** 0 **to** 64;
 - **type** result32 **is range** 31 **downto** 0;
 - **type** ttl **is range** 0.0 **to** 5.0;
 - **subtype** result16 **is** result32 **range** 15 **downto** 0;

User-defined enumeration types

■ Syntax

- **type** identifier **is** (element [,element]);

■ Examples

- **type** state **is** (idle, start, stop);
- **type** hexDigits **is** ('0', ..., '9', 'A', 'B', 'C', 'D', 'E', 'F');
- **type** std_logic **is** ('0', '1', 'U', 'X', 'Z', 'W', 'L', 'H', '-');
- Defined in package ieee.std_logic_1164

orGateSTD

```
library ieee;
use ieee.std_logic_1164.all;

entity orGateSTD is
  port ( a, b: in std_logic; c: out std_logic );
end orGateSTD;

architecture arch1 of orGateSTD is
begin
  c <= a or b;
end arch1;

architecture arch2 of orGateSTD is
begin
  c <= '1' when (a = '1' or b = '1') else '0';
end arch2;
```

- Values provided by std_logic
 - '0' – logical zero
 - '1' – logical one
 - 'U' – uninitialized
 - 'X' – unknown
 - 'Z' – high impedance
 - 'W' – weak unknown
 - 'L' – weak low
 - 'H' – weak high
 - '-' – don't care
- Compared to data type “bit”, std_logic allows more realistic VHDL designs
- Is there a difference between the two implementations?

Examples – OR Gate (using std_logic and arch1)

Albert-Ludwigs-Universität Freiburg



a / b	0	1	U	X	Z	W	L	H	-
0	0	1	U	X	X	0	0	1	0
1	1	1	1	1	1	1	1	1	1
U	U	1	U	X	X	X	X	1	X
X	X	1	X	X	X	X	X	1	X
Z	X	1	X	X	X	X	X	1	X
W	0	1	X	X	X	X	X	1	X
L	0	1	X	X	X	X	0	1	X
H	1	1	1	1	1	1	1	1	1
-	0	1	X	X	X	X	X	1	X

Examples – OR Gate (using std_logic and arch2)

Albert-Ludwigs-Universität Freiburg



a / b	0	1	U	X	Z	W	L	H	-
0	0	1	0	0	0	0	0	0	0
1	1	1	1	1	1	1	1	1	1
U	0	1	0	0	0	0	0	0	0
X	0	1	0	0	0	0	0	0	0
Z	0	1	0	0	0	0	0	0	0
W	0	1	0	0	0	0	0	0	0
L	0	1	0	0	0	0	0	0	0
H	0	1	0	0	0	0	0	0	0
-	0	1	0	0	0	0	0	0	0

User-defined arrays

■ Syntax

- **type** identifier **is array** (range [,range]) **of** element_type;

■ Examples

- **type** myVarArray **is array** (15 **downto** 0) **of** integer;
- **type** myBitArray **is array** (0 **to** 7) **of** bit;
- **type** my4x3Array **is array** (1 **to** 4, 1 **to** 3) **of** std_logic;

Some remarks

- VHDL is a strongly typed language
 - **type t1 is range 1 to 64;**
 - **type t2 is range 1 to 64;**

⇒ t1 and t2 are different data types!
- Packages such as `ieee.std_logic_1164` and `ieee.std_logic_arith` provide various conversion routines
- Some data types and so called attributes have been left out in this overview
 - natural, positive, record, access, ...
 - base, length, event, pos, succ, pred, leftof, ...

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

VHDL supports different classes of operators:

- 1 Logical operators
- 2 Relational operators
- 3 Shift operators
- 4 Addition operators
- 5 Unary operators
- 6 Multiplying operators
- 7 Miscellaneous operators

Order of precedence is highest for class 7 operators, followed by class 6 with the lowest precedence for class 1

Logical operators

- **and, or, nand, nor, xor, xnor**

Relational operators

- **=**: equal
- **/=**: not equal
- **<**: smaller than
- **<=**: smaller than or equal
- **>**: greater than
- **>=**: greater than or equal

Entity & Architecture

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity smallerThan is  
  port ( a, b: out std_logic );  
end smallerThan;  
  
architecture behavior of smallerThan is  
  signal cnt: integer range 0 to 10 := 5;  
begin  
  a <= '1' when (cnt <= 5) else '0';  
  b <= '1' when (cnt <= 3) else '0';  
end behavior;
```


Shift operators (on any one-dimensional array type with elements of type bit or Boolean)

- **sll**: shift left logical (fill right vacated bits with 0)
- **srl**: shift right logical (fill left vacated bits with 0)
- **sla**: shift left arithmetic (fill right vacated bits with rightmost bit)
- **sra**: shift right arithmetic (fill left vacated bits with leftmost bit)
- **rol**: rotate left (circular)
- **rор**: rotate right (circular)

Entity & Architecture

```
entity shiftLeftLogical is  
  port ( a: in bit_vector (5 downto 0); b: out bit_vector (5 downto 0) );  
end shiftLeftLogical;  
  
architecture behavior of shiftLeftLogical is  
begin  
  b <= a sll 1;  
end behavior;
```

Addition operators (require IEEE packages `std_logic_1164` and `std_logic_arith` / `std_logic_unsigned`)

- `+`: addition (on operands of any numeric type)
- `-`: subtraction (on operands of any numeric type)
- `&`: concatenation of two vectors

Unary operators (used to specify the sign of a numeric type)

- `+`: identity
- `-`: negation

Multiplying operators

- *: multiplication (on operands of any numeric type)
- /: division (on operands of any numeric type)
- **mod**: modulus (any integer type)
- **rem**: remainder (any integer type)

Miscellaneous operators

- **abs**: absolute value (any numeric type)
- **not**: logical negation (any bit or Boolean type)
- **: Exponentiation (floating/integer or integer/integer)

Entity & Architecture of multiplication

```
entity multiplication is  
  port ( a, b: in integer; c: out integer );  
end multiplication;  
  
architecture behavior of multiplication is  
begin  
  c <= a * b;  
end behavior;
```

Entity & Architecture of division

```
entity division is  
  port ( a, b: in integer; c: out integer );  
end division;  
  
architecture behavior of division is  
begin  
  c <= a / b;  
end behavior;
```

Operators – Example

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

The screenshot displays the Quartus II software interface. The main window shows the 'Compilation Report' for a project named 'multiplication'. The report is titled 'Flow Summary' and lists various compilation metrics. A red circle highlights the 'Timing Models' section, which indicates that the design is fully constrained for both setup and hold requirements.

Flow Status	Successful - Thu Mar 10 09:51:59 2011
Quartus II Version	10.1.0.ald 197.01/19/2011 SP 1.5J Web Edition
Revision Name	multiplication
Top-level Entity Name	multiplication
Family	EP2K10K10
Device	EP2K10K10-10
Timing Models	Final
Total logic elements	29 / 18,752 (< 1 %)
Total combinational functions	29 / 18,752 (< 1 %)
Dedicated logic registers	0 / 18,752 (0 %)
Total registers	0
Total multipliers	0
Total logic ports	0
Total memory bits	0 / 239,616 (0 %)
Embedded Multiplier 9-bit elements	6 / 52 (12 %)
Total PLLs	0 / 4 (0 %)

The 'Type Message' window at the bottom shows the following information:

- Info: Design is not fully constrained for setup requirements
- Info: Design is not fully constrained for hold requirements
- Info: Quartus II Assembler was successful. 0 errors, 0 warnings
- Info: Quartus II TimeQuest Timing Analyzer was successful. 0 errors, 4 warnings
- Info: Quartus II Full Compilation was successful. 0 errors, 14 warnings

Operators – Example

Albert-Ludwigs-Universität Freiburg



Quartus II - C:\Quartus\division\division - division

File Edit View Project Assignments Processing Tools Window Help

Project Navigator: division.vhd

Table of Contents

- Flow Summary
- Flow Settings
- Flow Non-Default Global Settings
- Flow Elapsed Time
- Flow OS Summary
- Flow Log
- Analysis & Synthesis
- Fitter
- Assembler
- TimeQuest Timing Analyzer

Compilation Report

Flow Summary

Flow Status	Successful - Thu Mar 10 09:54:59 2011
Quartus II Version	10.1.0.aid 197 01/19/2011 SP 1.5J Web Edition
Revision Name	division
Top-level Entity Name	division
Family	
Device	EP2C20Q2-40C8
Timing Models	Final
Total logic elements	1,214 / 18,752 (6 %)
Total combinational functions	1,214 / 18,752 (6 %)
Dedicated logic registers	0 / 18,752 (0 %)
Total registers	0
Total virtual pins	0
Total memory bits	0 / 239,616 (0 %)
Embedded Multiplier 9-bit elements	0 / 52 (0 %)
Total PLLs	0 / 4 (0 %)

Type Message

- Info: The selected device family is not supported by the report_metastability command.
- Info: Design is not fully constrained for setup requirements
- Info: Design is not fully constrained for hold requirements
- Info: Quartus II TimeQuest Timing Analyzer was successful. 0 errors, 4 warnings
- Info: Quartus II Full Compilation was successful. 0 errors, 10 warnings

System / Processing (95) / Extra Info (85) / Warning (7) / Critical Warning (3) / Error / Suppressed (6) / Flag

Message: 0 of 314

100% 00:00:37

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

Constants

- Can be of any data type
- Cannot be changed or written to
- Examples
 - **constant** PI: real := 3.1415;
 - **constant** PERIOD: time := 100 ns;
 - **type** vecType **is array (0 to 3) of integer;**
constant VEC: vecType := (2,4,-1,7);

Variables

- Like variables in (other) programming languages
- Used to store temporary values
- Have to be declared within processes and are only visible in this scope
- Are updated immediately without any delay
- Examples
 - Declaration
 - **variable** var1: boolean := false;
 - **variable** var2: integer **range** 0 to 16 := 4;
 - **type** var3Type **is array** (3 **downto** 0) **of** std_logic;
 - **variable** var3: var3Type;
 - Assignment
 - var1 := true;
 - var2 := var2 + 6;
 - var3(2) := 'X';

Signals

- Represent a wire or register value
- Can be of any data type
- Can be declared in architectures only
- Have a time delay associated with them
 - user-specified, e.g. "**after** 10 ns"
 - small delta delay
- Examples
 - **signal** sum: std_logic;
 - **signal** clk: bit;
 - **signal** data: std_logic_vector (0 to 7) := "00X0X011";
 - **signal** value: integer **range** 16 to 31 := 17;

Simple signal assignments

- `sum <= (a xor b) after 2 ns;`
- `data(1) <= 'X';` — implicit delta delay.
- `clk <= '0', '1' after 5 ns, '0' after 10 ns, '1' after 15 ns;`

Conditional signal assignments

- **when-else**
- **with-select**

Constants, Variables & Signals – Example

Albert-Ludwigs-Universität Freiburg



Entity & Architecture of clock

```
library ieee;  
use ieee.std_logic_1164.all;  
entity clock is  
  port ( clk: out std_logic );  
end clock;  
  
architecture behavior of clock is  
begin  
  clk <= '0', '1' after 5 ns, '0' after 10 ns, '1' after 15 ns;  
end behavior;
```

Constants, Variables & Signals – RTL Simulation

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

The screenshot displays the ModelSim ALTERA STARTER EDITION 6.6d interface. The main window shows a simulation wave for the signal `/clock_vhd_tst/clock`. The wave is a square wave with a period of 10,000 ps, starting at 0 ps and ending at 30,000 ps. The cursor is positioned at 0 ps. The transcript window at the bottom shows the following commands:

```
# Loading ieee.std_logic_1164(body)
# Loading work.clock_vhd_tst(clock_arch)
# Loading work.clock(behavior)
#
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run -all

V$SM 2>
```

The status bar at the bottom indicates the simulation time is 30 ns, the delta is 1, and the current time is 0 ps to 31500 ps. The system tray shows the time as 13:44.

Constants, Variables & Signals – Gate-Level Sim.

Albert-Ludwigs-Universität Freiburg



The screenshot shows the ModelSim ALTERA STARTER EDITION 6.6d interface. The main window displays a simulation wave for a signal named 'clock_vhd_tst/clock'. The wave is currently flat at 0 ps. The transcript window at the bottom shows the following text:

```
ModelSim ALTERA STARTER EDITION 6.6d
File Edit View Compile Simulate Add Wave Tools Layout Window Help
Layout Simulate ColumnLayout Default
Wave
Name: clock_vhd_tst/clock
Time: 0 ps
Cursor 1: 0 ps
Transcript
# Loading timing data from clock_vhd_tst.do
# ** Note: (vsim-3587) SDF Backannotation Successfully Completed.
# Time: 0 ps Iteration: 0 Region: /clock_vhd_tst File: C:/Quartus/aside70/simulation/modelsim/clock_vht
#
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.structure
# view signals
# .main_pane.objects.interior.cs.body.tree
# run -all
v$M 2>
Now: 30 ns Delta: 1 sim:/clock_vhd_tst 0 ps to 31500 ps 13:45
```

A red underline is drawn under the text "Non-synthesizable VHDL code!" in the transcript window.

Constants, Variables & Signals – Example

Albert-Ludwigs-Universität Freiburg



Entity

```
entity mux4to1 is  
  port ( i3, i2, i1, i0: in bit;  
         sel: in bit_vector (1 downto 0);  
         otp: out bit );  
end mux4to1;
```

when-else

```
architecture wElse of mux4to1 is  
begin  
  otp <= i0 when sel = "00" else  
    i1 when sel = "01" else  
    i2 when sel = "10" else  
    i3;  
end wElse;
```

with-select

```
architecture wSelect of mux4to1 is  
begin  
  with sel select  
    otp <= i0 when "00",  
    i1 when "01",  
    i2 when "10",  
    i3 when others ;  
end wSelect;
```


when-else

- Specifies a logic function in the form of a truth table

with-select


- Choices can express
 - single values, e.g. ... **when** "01"
 - a range, e.g. ... **when** 51 **to** 60
 - combined choices, e.g. ... **when** "00" **or** "01" **or** "11"
- No two choices are allowed to overlap
- All possible values of the "choice expression" have to be covered by the set of choices (unless an **others** choice is present)

Both **when-else** and **with-select** cannot be used inside a process!

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 **Entities & architectures**
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

Each VHDL design is based on two parts

 - An entity defining the system's interface
- An architecture describing an entity's implementation



The entity describes the interface of a digital system:

```
entity name_of_entity is  
  [ generic ( parameter list ); ]  
  [ port ( I/O pins ); ]  
  [ begin assertions to be checked; ]  
end [ entity ] [ name_of_entity ];
```

- Generic declarations are optional and determine local constants used for e.g. sizing the entity (bus widths, ...)
- Assertions are optional and can be used to perform consistency checks

“Empty” entity

```
entity test is  
end test;
```

D-Flipflop

```
library ieee;  
use ieee.std_logic_1164.all;  
entity flipflop is  
  port ( data, clk, set, reset: in std_logic; q: out std_logic );  
end flipflop;
```

8-bit 4-to-1 multiplexer

```
library ieee;
use ieee.std_logic_1164.all;

entity mux_4_to_1_8bit is
  port
  (
    i3, i2, i1, i0: in std_logic_vector (7 downto 0);
    sel: in std_logic_vector (1 downto 0);
    otp: out std_logic_vector (7 downto 0)
  );
end mux_4_to_1_8bit;
```

n-bit 4-to-1 multiplexer

```
library ieee;
use ieee.std_logic_1164.all;

entity mux_4_to_1_nbit is
  generic ( n: positive );
  port
  (
    i3, i2, i1, i0: in std_logic_vector (n-1 downto 0);
    sel: in std_logic_vector (1 downto 0);
    otp: out std_logic_vector (n-1 downto 0)
  );
end mux_4_to_1_nbit;
```

The architecture defines the implementation of an entity:

```
architecture name_of_architecture of name_of_entity is  
  -- Declarations like ...  
    -- component declarations  
    -- type declarations  
    -- signal declarations  
    -- constant declarations  
    -- function declarations  
    -- procedure declarations  
begin  
  -- Statements, processes, ...  
end name_of_architecture;
```


Statements within an architecture are executed in parallel!

Entity

```
entity halfAdder is  
  port ( a, b: in bit; sum, cout: out bit );  
end halfAdder;
```

Architecture arch1

```
architecture arch1 of halfAdder is  
begin  
  sum <= a xor b;  
  cout <= a and b;  
end arch1;
```

Architecture arch2

```
architecture arch2 of halfAdder is  
begin  
  cout <= a and b;  
  sum <= a xor b;  
end arch2;
```

⇒ arch1 and arch2 describe the same behavior!

D-Flipflop

```
library ieee;  
use ieee.std_logic_1164.all;  
entity flipflop is  
  port ( data, clk, set, reset: in std_logic; q: out std_logic );  
end flipflop;  
architecture behavior of flipflop is  
begin  
  process ( clk, set, reset )  
  begin  
    if reset = '1' then  
      q <= '0';  
    elsif set = '1' then  
      q <= '1';  
    elsif (clk'event and clk = '1') then  
      q <= data;  
    end if;  
  end process;  
end behavior;
```

8-bit 4-to-1 multiplexer

```
library ieee;
use ieee.std_logic_1164.all;

entity mux_4_to_1_8bit is
  port
    ( i3, i2, i1, i0: in std_logic_vector (7 downto 0);
      sel: in std_logic_vector (1 downto 0);
      otp: out std_logic_vector (7 downto 0) );
end mux_4_to_1_8bit;

architecture behavior of mux_4_to_1_8bit is
begin
  process ( i3, i2, i1, i0, sel )
  begin
    if sel = "11" then otp <= i3;
    elsif sel = "10" then otp <= i2;
    elsif sel = "01" then otp <= i1;
    elsif sel = "00" then otp <= i0;
    end if;
  end process;
end behavior;
```

XNOR Gate


```
library ieee;  
use ieee.std_logic_1164.all;  
entity xnorGate is  
  port ( a, b : in std_logic; c : out std_logic );  
end xnorGate;  
architecture behavior of xnorGate is  
  signal x, y : std_logic;  
begin  
  x <= (a and b) after 5 ns;  
  y <= ((not a) and (not b)) after 10 ns;  
  c <= (x or y) after 5 ns;  
end behavior;  
  
-- The VHDL statements given above are executed in parallel!  
-- Signal assignments are executed concurrently!  
-- Changing the order does not matter!
```

Entities & Architectures – RTL Simulation

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

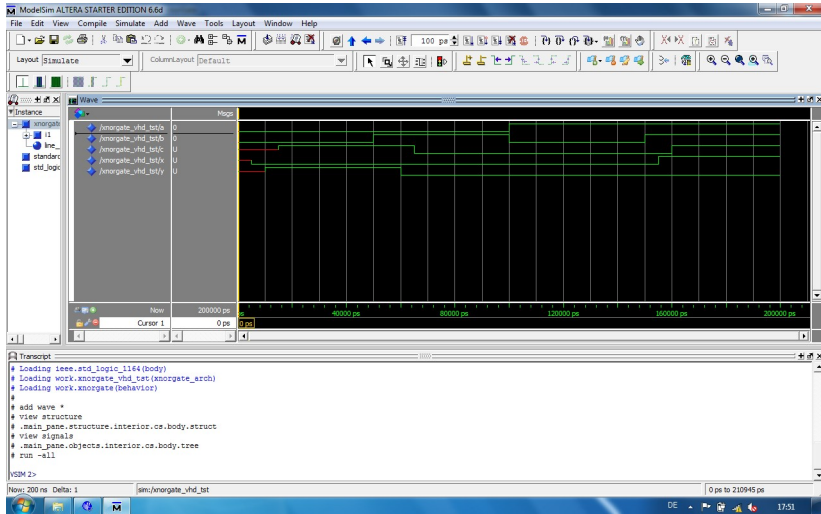



Entities & Architectures – Gate-Level Simulation

Albert-Ludwigs-Universität Freiburg



UNI
FREIBURG

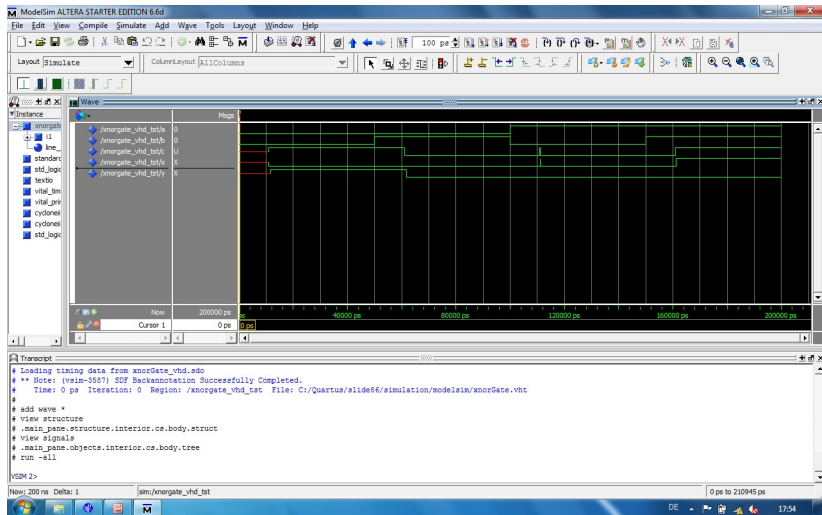


 

- The architecture can be structural, behavioral, or mixed
 - Structural descriptions use component instances
 - Behavioral descriptions describe the behavior of a digital system without defining its structure
- Structural hierarchy is essential for a compact and clear modeling of large systems
- In hierarchical designs, mixing structural and behavioral descriptions is mandatory (at least for the “leafs” in the hierarchy)

Entities & Architectures – Examples

Albert-Ludwigs-Universität Freiburg

 


4-Bit Shift Register – Entity

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity shift_register_4bit is  
    port ( din, clk, set, reset: in std_logic; dout: out std_logic );  
end shift_register_4bit;
```


Entities & Architectures – Examples

Albert-Ludwigs-Universität Freiburg

 

4-Bit Shift Register – Architecture

```
architecture structural of shift_register_4bit is  
  component flipflop  
    port ( data, clk, set, reset: in std_logic; q: out std_logic );  
  end component;  
  signal T: std_logic_vector (2 downto 0);  
begin  
  bit3: flipflop port map ( din, clk, set, reset, T(2) );  
  bit2: flipflop port map ( T(2), clk, set, reset, T(1) );  
  bit1: flipflop port map ( T(1), clk, set, reset, T(0) );  
  bit0: flipflop port map ( T(0), clk, set, reset, dout );  
end structural;
```

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 **Components & configurations**
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

As demonstrated in the previous example, hierarchical VHDL designs combine “basic building blocks” (entities and their associated architectures) to form new designs

- **component** describes the interface of an entity that will be used as an instance in the current design
- **port map** describes the interconnection between components, which can be realized in two ways
 - Positional association
 - Explicit association

⇒ Architectures and their components can define a hierarchy of arbitrary depth!

Components & Configurations


Positional vs. Explicit Association

Albert-Ludwigs-Universität Freiburg



Entity
 
```
entity fullAdder is  
  port ( a, b, cin: in bit;  
         sum, cout: out bit );  
end fullAdder;
```



Architecture


```
architecture structure of fullAdder is  
  component halfAdder port ( a, b: in bit; sum, cout: out bit ); end component;  
  component orGate port ( a, b: in bit; c: out bit ); end component;  
  signal x, y, z: bit;  
begin  
  i1: halfAdder port map ( a, b, x, y ); -- positional.  
  i2: halfAdder port map ( sum => sum, a => x, cout => z, b => cin ); -- explicit.  
  o1: orGate port map ( y, z, cout );  
end structure;
```

VHDL specification = entity + architecture(s)

- Each entity requires at least one architecture
- Multiple architectures can be defined for a single entity
 - Allows designers to use different implementations without changing the interface
 - Mapping an architecture to a particular component can be done via **configuration** statements
- By default, the most recently analyzed architecture is used

Components & Configurations – Example

Albert-Ludwigs-Universität Freiburg

 

test


```
library ieee;
use ieee.std_logic_1164.all;

entity test is
    port ( a, b, c, d: in std_logic; x, y: out std_logic );
end test;

architecture structure of test is
    component orGate
        port ( a, b: in std_logic; c: out std_logic );
    end component;
begin
    o1: orGate port map ( a, b, x );
    o2: orGate port map ( c, d, y );
end structure;
```

Components & Configurations – Example

Albert-Ludwigs-Universität Freiburg

 

orGate

```
library ieee;
use ieee.std_logic_1164.all;


entity orGate is
  port ( a, b: in std_logic; c: out std_logic );
end orGate;

architecture ok of orGate is
begin
  c <= a or b;
end ok;

architecture faulty of orGate is
begin
  c <= a and b;
end faulty;
```

Components & Configurations – Example

Albert-Ludwigs-Universität Freiburg

 

orGate

```
library ieee;
use ieee.std_logic_1164.all;

entity orGate is
    port ( a, b: in std_logic; c: out std_logic );
end orGate;

architecture ok of orGate is
begin
    c <= a or b;
end ok;

architecture faulty of orGate is
begin
    c <= a and b;
end faulty; -- default configuration!
```


Components & Configurations – Example

Albert-Ludwigs-Universität Freiburg



test

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity test is  
  port ( a, b, c, d: in std_logic; x, y: out std_logic );  
end test;  
  
architecture structure of test is  
  component orGate  
    port ( a, b: in std_logic; c: out std_logic );  
  end component;  
begin  
  o1: orGate port map ( a, b, x );  
  o2: orGate port map ( c, d, y );  
end structure;
```

configuration 1

```
configuration cfg1 of test is  
  for structure  
    for all: orGate use entity work.orGate(ok); end for;  
  end for;  
end cfg1;
```

Components & Configurations – Example

Albert-Ludwigs-Universität Freiburg



test

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity test is  
  port ( a, b, c, d: in std_logic; x, y: out std_logic );  
end test;  
  
architecture structure of test is  
  component orGate  
    port ( a, b: in std_logic; c: out std_logic );  
  end component;  
begin  
  o1: orGate port map ( a, b, x );  
  o2: orGate port map ( c, d, y );  
end structure;
```

configuration 2 (not the intended functionality, but possible!)

```
configuration cfg2 of test is  
  for structure  
    for o1: orGate use entity work.orGate(ok); end for;  
    for o2: orGate use entity work.orGate(faulty); end for;  
  end for;  
end cfg2;
```

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 **Processes**
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

Behavioral VHDL descriptions usually consist of a set of concurrently executed processes:

```
[ process_label: ] process [ ( sensitivity_list ) ] [ is ]  
  -- constants & variables used inside the process have to be defined here.  
begin  
  -- list of sequential statements such as:  
  -- signal & variable assignments  
  -- if statement  
  -- case statement  
  -- loop statement  
  -- null statement  
  -- wait statement  
  -- ...  
end process [ process_label ];
```

- While all processes of a design are executed **concurrently**, the statements within a single process are executed **sequentially** in the order they are written
- No hierarchy of processes allowed in VHDL
- Only simple signal assignments allowed inside a process
- When a simulation starts, each process will be executed once
- Afterwards, processes will be reactivated according to events regarding signals of the associated sensitivity list
- Processes are mainly used to describe sequential circuits (e.g. the DFF shown on Slide 84), but not necessarily

Signal assignments outside processes can be viewed as implicit processes!

Entity

```
entity halfAdder is  
  port ( a, b: in bit; sum, cout: out bit );  
end halfAdder;
```

Architecture arch1

```
architecture arch1 of halfAdder is  
begin  
  cout <= a and b;  
  sum <= a xor b;  
end arch1;
```

Architecture arch2

```
architecture arch2 of halfAdder is  
begin  
  process ( a, b )  
  begin  
    cout <= a and b;  
  end process;  
  process ( a, b )  
  begin  
    sum <= a xor b;  
  end process;  
end arch2;
```

⇒ Again, arch1 and arch2 describe the same behavior!

Full Adder

```
library ieee;
use ieee.std_logic_1164.all;

entity fullAdder is
  port ( a, b, cin: in std_logic; sum, cout: out std_logic );
end fullAdder;

architecture behavior of fullAdder is
  signal i1, i2: std_logic;
begin

  P1: process ( a, b ) -- P1 defines the 1st half adder.
  begin
    i1 <= a xor b after 10 ns;
    i2 <= a and b after 10 ns;
  end process;

  P2: process ( i1, i2, cin ) -- P1 defines the 2nd half adder plus the OR gate.
  begin
    sum <= i1 xor cin;
    cout <= i2 or (i1 and cin);
  end process;


end behavior;
```

Processes – RTL Simulation

Albert-Ludwigs-Universität Freiburg




UNI
FREIBURG

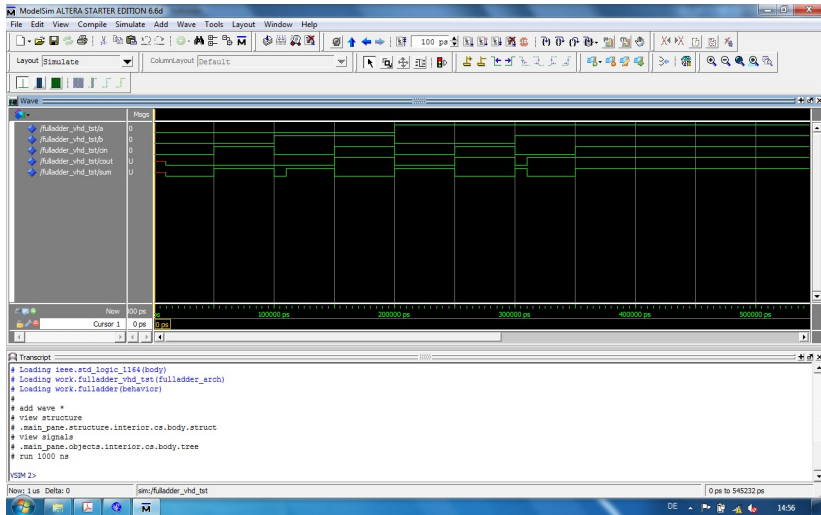

Processes – Gate-Level Simulation

Albert-Ludwigs-Universität Freiburg

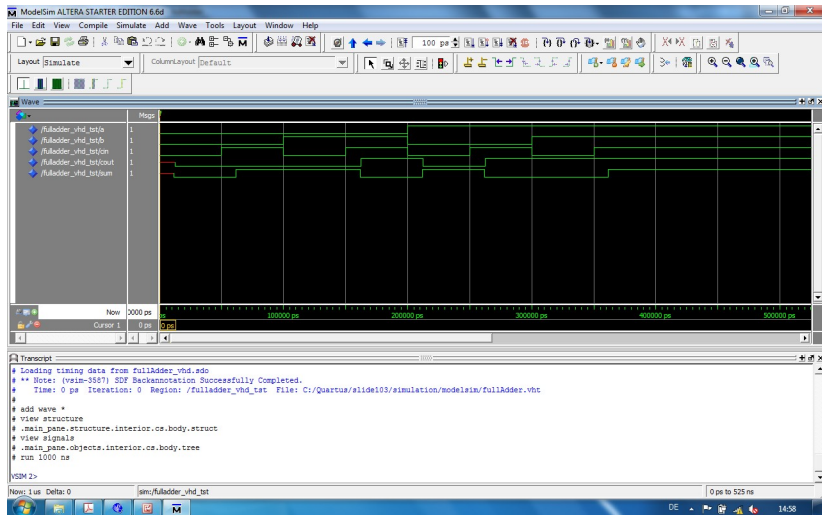

Clock generator (not synthesizable, but often used in testbenches!)

```
entity clock is  
  port ( clk: out bit );  
end clock;
```

```
architecture behavior of clock is  
begin  
  process  
    begin  
      clk <= '0';  
      wait for 10 ns;  
      clk <= '1';  
      wait for 10 ns;  
    end process;  
end behavior;
```

Testbench for the full adder using clocks.

```
...  
  
process  
begin  
  a <= '0'; wait for 160 ns;  
  a <= '1'; wait for 160 ns;  
end process;  
  
process  
begin  
  b <= '0'; wait for 80 ns;  
  b <= '1'; wait for 80 ns;  
end process;  
  
process  
begin  
  cin <= '0'; wait for 40 ns;  
  cin <= '1'; wait for 40 ns;  
end process;  
  
...
```

Sensitivity lists are a shorthand for a single **wait on**-statement at the end of the process body

Sensitivity list

```
process ( a, b )  
begin  
  c <= a and b;  
end process;
```

is equivalent to

wait on-Statement

```
process  
begin  
  c <= a and b;  
  wait on a, b;  
end process;
```

- VHDL supports different types of **wait**-statements
 - **wait on** signal_list
 - Wait until at least one of the signals in signal_list changes
 - Example: **wait on** a, b;
 - **wait until** condition
 - Wait until condition is met
 - Example: **wait until** (clk'event **and** clk = '1');
 - **wait for** duration
 - Wait for specified amount of time
 - Example: **wait for** 25 ns;
 - **wait**
 - Suspend indefinitely
- If no sensitivity list is specified, a **wait**-statement has to be included to ensure that the process will stop
- It is not allowed to have both sensitivity lists and **wait**-statements

Other “sequential” statements that can be used inside processes

- **if**
- **case**
- **loop, while-loop, for-loop**
- **null**

Except for **if** and **case**...

- None of the above statements are synthesizable
- Most of them are used for testing

if-statement

- Comparable to if-statements in other programming languages

8-bit 4-to-1 multiplexer

...

```
process ( i3, i2, i1, i0, sel )
```

```
begin
```

```
  if sel = "11" then otp <= i3;
```

```
  elsif sel = "10" then otp <= i2;
```

```
  elsif sel = "01" then otp <= i1;
```

```
  elsif sel = "00" then otp <= i0;
```

```
  end if;
```

```
end process;
```

...

case-statement

- Executes one of several sequences of statements, based on a single expression to be evaluated
- Choices can be
 - single values, e.g. ... **when** "01"
 - a range, e.g. ... **when** 51 **to** 60
 - combined choices, e.g. ... **when** "00" **or** "01" **or** "11"
- No two choices are allowed to overlap
- If there is no **when others**-statement, all possible values of the expression have to be covered by the set of choices

Temperature

```
entity temperature is  
  port ( val: in integer range 0 to 100; a, b, c, d: out bit );  
end temperature;  
  
architecture behavior of temperature is  
begin  
  process ( val )  
  begin  
    a <= '0'; b <= '0'; c <= '0'; d <= '0';  
    case val is  
      when 51 to 60 => a <= '1';  
      when 61 to 70 => b <= '1';  
      when 71 to 80 => c <= '1';  
      when others => d <= '1';  
    end case;  
  end process;  
end behavior;
```

loop-statements

■ loop

- Requires a **wait**-statement
- Executed continuously until an **exit** is encountered

■ while-loop

- Requires a **wait**-statement
- Executed as long as the “iteration condition” is true

■ for-loop

- Uses an integer iteration scheme, determining the number of iterations

■ All three variants can be combined with...

- **next**: terminates the rest of the current loop iteration; execution will proceed to the next loop iteration
- **exit**: terminates the loop entirely; continues with the next statement after the exited loop

Testbench for the full adder using **loop**

...

process

variable cnt: std_logic := '1';

variable num: integer := 0;

begin

loop

if cnt = '1' **then** cnt := '0'; **else** cnt := '1'; **end if**;

num := num + 1;

a <= cnt;

wait for 160 ns;

exit when num > 9;

end loop;

end process;

...

Testbench for the full adder using **while-loop**

```
...  
process  
  variable cnt: std_logic := '1';  
  variable num: integer := 0;  
begin  
  while num <= 9 loop  
    if cnt = '1' then cnt := '0'; else cnt := '1'; end if;  
    num := num + 1;  
    b <= cnt;  
    wait for 80 ns;  
  end loop;  
end process;  
...
```

Testbench for the full adder using **for-loop**

```
...  
  
process  
  variable cnt: std_logic := '1';  
begin  
  for num in 1 to 9 loop  
    if cnt = '1' then cnt := '0'; else cnt := '1'; end if;  
    cin <= cnt;  
    wait for 40 ns;  
  end loop;  
end process;  
  
...
```

null-statement

- States that no action will occur
- Useful as part of **case**-statements where all choices must be covered, even if some of them can be ignored

Example

```
-- Assumptions:  
-- 1) 'val' is an integer, ranging from 0 to 7.  
-- 2) If 'val' is equal to 0|1|3|4|6|7, nothing has to be done.  
-- 3) 'c' is an output, while 'a' and 'b' are inputs.  
...
```

```
process ( val )  
begin  
  case val is  
    when 2 or 5 => c <= a xor b;  
    when others => null;  
  end case;  
end process;
```

```
...
```

Variable vs. signal assignments inside processes

- A **variable** changes instantaneously when the corresponding variable assignment is executed (without any time delay)
- A **signal** changes a delay after the assignment expression is executed (user-specified or delta delay)
 - ⇒ All signal assignments inside a process are sequentially evaluated until the process is stopped and are performed in parallel afterwards

Example of a process using variables

```
architecture var of example is  
  signal trigger: integer := 0;  
  signal rst: integer := 0;  
begin  
  process  
    variable var1: integer := 1;  
    variable var2: integer := 2;  
    variable var3: integer := 3;  
  begin  
    wait on trigger;  
    var1 := var2;  
    var2 := var1 + var3;  
    var3 := var2;  
    rst <= var1 + var2 + var3;  
  end process;  
end var;
```

- All variables are computed sequentially and their values are updated
- instantaneously after the 'trigger' signal arrives. Next, 'rst' is computed using
- the new values of 'var1..3' and is updated a delay delta after 'trigger' arrives.
- var1 = ?, var2 = ?, var3 = ?, rst = ?

Example of a process using variables

```
architecture var of example is  
  signal trigger: integer := 0;  
  signal rst: integer := 0;  
begin  
  process  
    variable var1: integer := 1;  
    variable var2: integer := 2;  
    variable var3: integer := 3;  
  begin  
    wait on trigger;  
    var1 := var2;  
    var2 := var1 + var3;  
    var3 := var2;  
    rst <= var1 + var2 + var3;  
  end process;  
end var;
```

- All variables are computed sequentially and their values are updated
- instantaneously after the 'trigger' signal arrives. Next, 'rst' is computed using
- the new values of 'var1..3' and is updated a delay delta after 'trigger' arrives.
- var1 = 2, var2 = 5, var3 = 5, rst = 12

Example of a process using signals

architecture sig of example is

signal trigger: integer := 0;

signal rst: integer := 0;

signal sig1: integer := 1;

signal sig2: integer := 2;

signal sig3: integer := 3;

begin

process

begin

wait on trigger;

sig1 <= sig2;

sig2 <= sig1 + sig3;

sig3 <= sig2;

rst <= sig1 + sig2 + sig3;

end process;

end sig;

- All signal assignments will be executed at the same time (event on 'trigger'),
- using the old values of 'sig1', 'sig2', 'sig3', but updated a delta time after
- 'trigger' has arrived.
- sig1 = ?, sig2 = ?, sig3 = ?, rst = ?

Example of a process using signals

architecture sig of example is

signal trigger: integer := 0;

signal rst: integer := 0;

signal sig1: integer := 1;

signal sig2: integer := 2;

signal sig3: integer := 3;

begin

process

begin

wait on trigger;

sig1 <= sig2;

sig2 <= sig1 + sig3;

sig3 <= sig2;

rst <= sig1 + sig2 + sig3;

end process;

end sig;

- All signal assignments will be executed at the same time (event on 'trigger'),
- using the old values of 'sig1', 'sig2', 'sig3', but updated a delta time after
- 'trigger' has arrived.
- sig1 = 2, sig2 = 4, sig3 = 2, rst = 6

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 **Parameterized hardware descriptions**
- 13 Semantics
- 14 Evaluation



VHDL provides a mechanism to easily describe parameterized hardware components

- Generic entities by including lists to define the **generic** constants that parameterize the entity
- Iterative component instantiation with **for-generate**
- Conditional component instantiation with **if-generate**

4-Bit Shift Register

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity shift_register_4bit is  
  port ( din, clk, set, reset: in std_logic; dout: out std_logic );  
end shift_register_4bit;  
  
architecture structural of shift_register_4bit is  
  component flipflop  
    port ( data, clk, set, reset: in std_logic; q: out std_logic );  
  end component;  
  signal T: std_logic_vector (2 downto 0);  
begin  
  bit3: flipflop port map ( din, clk, set, reset, T(2) );  
  bit2: flipflop port map ( T(2), clk, set, reset, T(1) );  
  bit1: flipflop port map ( T(1), clk, set, reset, T(0) );  
  bit0: flipflop port map ( T(0), clk, set, reset, dout );  
end structural;
```

n-Bit Shift Register

```
library ieee;
use ieee.std_logic_1164.all;

entity shift_register_nbit is
  port ( din, clk, set, reset: in std_logic; dout: out std_logic );
end shift_register_nbit;

architecture structural of shift_register_nbit is
  component flipflop
    port ( data, clk, set, reset: in std_logic; q: out std_logic );
  end component;
  signal T: std_logic_vector (2 downto 0);
begin
  bit3: flipflop port map ( din, clk, set, reset, T(2) );
  bit2: flipflop port map ( T(2), clk, set, reset, T(1) );
  bit1: flipflop port map ( T(1), clk, set, reset, T(0) );
  bit0: flipflop port map ( T(0), clk, set, reset, dout );
end structural;
```

n-Bit Shift Register

```
library ieee;
use ieee.std_logic_1164.all;

entity shift_register_nbit is
    generic ( n: positive );
    port ( din, clk, set, reset: in std_logic; dout: out std_logic );
end shift_register_nbit;

architecture structural of shift_register_nbit is
    component flipflop
        port ( data, clk, set, reset: in std_logic; q: out std_logic );
    end component;
    signal T: std_logic_vector (2 downto 0);
begin
    bit3: flipflop port map ( din, clk, set, reset, T(2) );
    bit2: flipflop port map ( T(2), clk, set, reset, T(1) );
    bit1: flipflop port map ( T(1), clk, set, reset, T(0) );
    bit0: flipflop port map ( T(0), clk, set, reset, dout );
end structural;
```


n-Bit Shift Register

```
library ieee;
use ieee.std_logic_1164.all;

entity shift_register_nbit is
    generic ( n: positive );
    port ( din, clk, set, reset: in std_logic; dout: out std_logic );
end shift_register_nbit;

architecture structural of shift_register_nbit is
    component flipflop
        port ( data, clk, set, reset: in std_logic; q: out std_logic );
    end component;
    signal T: std_logic_vector (n-2 downto 0);
begin
    bit3: flipflop port map ( din, clk, set, reset, T(2) );
    bit2: flipflop port map ( T(2), clk, set, reset, T(1) );
    bit1: flipflop port map ( T(1), clk, set, reset, T(0) );
    bit0: flipflop port map ( T(0), clk, set, reset, dout );
end structural;
```

n-Bit Shift Register

```
library ieee;
use ieee.std_logic_1164.all;

entity shift_register_nbit is
    generic ( n: positive );
    port ( din, clk, set, reset: in std_logic; dout: out std_logic );
end shift_register_nbit;

architecture structural of shift_register_nbit is
    component flipflop
        port ( data, clk, set, reset: in std_logic; q: out std_logic );
    end component;
    signal T: std_logic_vector (n-2 downto 0);
begin
    label1: for i in n-1 downto 0 generate
        label2: if i = n-1 generate
            bitL: flipflop port map ( din, clk, set, reset, T(n-2) ); end generate;
        label3: if i > 0 and i < n-1 generate
            bitM: flipflop port map ( T(i), clk, set, reset, T(i-1) ); end generate;
        label4: if i = 0 generate
            bitR: flipflop port map ( T(0), clk, set, reset, dout ); end generate;
        end generate;
end structural;
```

Component instantiation (in this example within a testbench)


```
...  
architecture arch of shift_register_nbit_vhd_tst is  
  ...  
  component shift_register_nbit  
    generic ( n : positive );  
    port ( din, clk, set, reset: in std_logic; dout: out std_logic );  
  end component;  
begin  
  i1: shift_register_nbit  
    generic map ( 7 ) --- Note, here is no semicolon!  
    port map ( din, clk, set, reset, dout );  
  ...  
end arch;
```

Parameterized Hardware Descriptions – RTL Sim.

Albert-Ludwigs-Universität Freiburg




UNI
FREIBURG

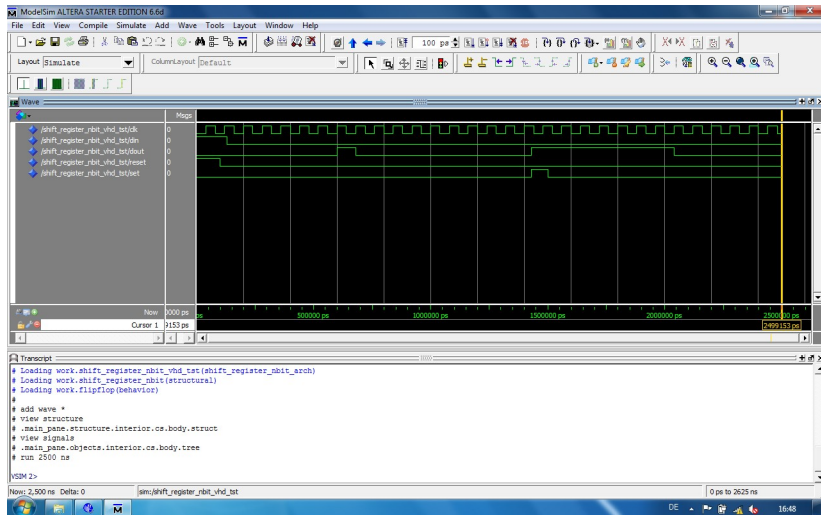

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 **Semantics**
- 14 Evaluation

Overview

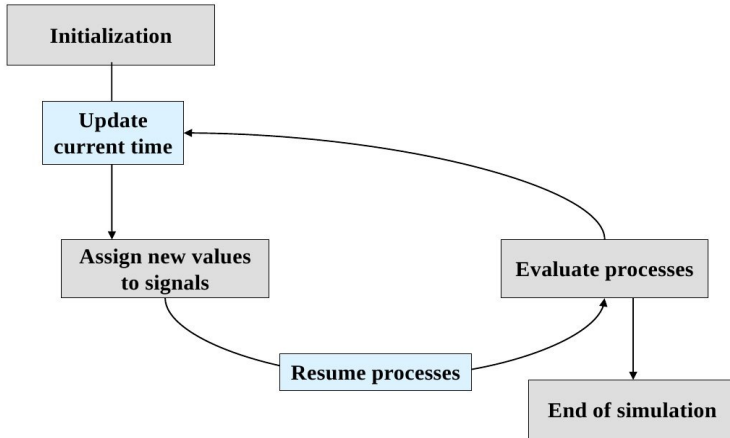- To define the semantics of VHDL, one can assume that the structural hierarchy of a design “is flattened” into a behavioral description
- Execution of VHDL models consists of an initialization phase followed by the repetitive execution of process statements
- A (simulation) step consists of two phases
 - Signal assignments
 - Execution of processes



Transaction list

- For signal assignments
- Entries of the form (s, v, t) , meaning “signal s is set to value v at time t ”

Process activation list

- For reactivating processes
- Entries of the form (p, t) , meaning “process p resumes at time t ”

Initialization

- At the beginning of the simulation, the current time t_{curr} is assumed to be 0 ns
- An initial value is assigned to each signal
 - Default value (if specified)
 - First value in enumeration based types
 - The initial value is assumed to have been the value of the particular signal for an infinite length of time prior to the start of the simulation

Initialization

- During the initialization phase each process is executed once (until it suspends)
- Signal assignments stated inside processes are collected in the transaction list (the statements get evaluated, but the corresponding signals are not updated immediately!)
- After the initialization, the time of the next simulation cycle is calculated: $t_{next} = \min(t_1, t_2, t_3)$ with
 - 1 t_1 : time'high (end of simulation time)
 - 2 t_2 : earliest time in transaction list (if non-empty)
 - 3 t_3 : earliest time in process activation list (if non-empty)

Example

architecture behavior **of** semantics **is**

signal a : std_logic := '0';

signal b : std_logic := '1';

signal c : std_logic := '1';

signal d : std_logic := '0';

begin

swap1: **process** (a, b)

begin

a <= b **after** 10 ns;

b <= a **after** 10 ns;

end process swap1;

swap2: **process**

begin

c <= d;

d <= c;

wait for 15 ns;

end process swap2;

end behavior;

“Update current time” / “Assign new values to signals”

- Each simulation cycle starts with setting the current time to the next time at which changes must be considered:

$$t_{curr} = t_{next}$$

- For all (s, v, t_{curr}) in the transaction list
 - Remove (s, v, t_{curr}) from the list
 - Set s to value v
- For all processes p waiting on signal s (**wait on**)
 - Insert (p, t_{curr}) into the process activation list
 - Similarly, if condition of a **wait until**-statement changes its value

Example

architecture behavior **of** semantics **is**

signal a : std_logic := '0';

signal b : std_logic := '1';

signal c : std_logic := '1';

signal d : std_logic := '0';

begin

swap1: **process** (a, b)

begin

a <= b **after** 10 ns;

b <= a **after** 10 ns;

end process swap1;

swap2: **process**

begin

c <= d;

d <= c;

wait for 15 ns;

end process swap2;

end behavior;

“Resume processes” / “Evaluate processes”

- Resume all processes p with entries (p, t_{curr}) in the process activation list
- Execute all activated processes “in parallel”, i.e. in arbitrary order
- Signal assignments are collected in the transaction list (again, the corresponding signals are not updated immediately!)
 - $s \leftarrow a$ **and** b ; \Rightarrow insert $(s, a \wedge b, t_{curr})$
 - $clk \leftarrow '0'$ **after** 10ns; \Rightarrow insert $(clk, 0, t_{curr} + 10\text{ns})$

“Resume processes” / “Evaluate processes”

- Processes are executed until a **wait**-statement is encountered
- If process p stops at a **wait for**-statement, then update the process activation list
 - “ p stops at **wait for** 20 ns” \Rightarrow insert $(p, t_{curr} + 20\text{ns})$
- When all processes have stopped, the time of the next simulation cycle is calculated: $t_{next} = \min(t_1, t_2, t_3)$ with
 - 1 t_1 : time'high (end of simulation time)
 - 2 t_2 : earliest time in transaction list (if non-empty)
 - 3 t_3 : earliest time in process activation list (if non-empty)
- Simulation terminates, if t_{next} is equal to time'high and both the transaction list and the process activation list are empty

Example

architecture behavior **of** semantics **is**

signal a : std_logic := '0';

signal b : std_logic := '1';

signal c : std_logic := '1';

signal d : std_logic := '0';

begin

swap1: **process** (a, b)

begin

a <= b **after** 10 ns;

b <= a **after** 10 ns;

end process swap1;

swap2: **process**

begin

c <= d;

d <= c;


wait for 15 ns;

end process swap2;

end behavior;


Delta delay

 - Time does not necessarily proceed between two (simulation) steps
 - Several (potentially an infinite number of) steps can take place at the same time t_{curr}
- ⇒ Signal assignments which take place at the same time in two consecutive steps are separated by one delta delay



Simulation time does not proceed due to delta delays!

Current time	Delta delay	Event
0 ns	1	-- evaluation of inverter -- (A, 1, 0 ns)

 

Simulation time does not proceed due to delta delays!

Current time	Delta delay	Event
0 ns	1	-- evaluation of inverter -- (A, 1, 0 ns)
	2	-- evaluation of AND and NAND -- (B, 0, 0ns), (C, 1, 0ns)
	3	-- evaluation of AND -- (C, 0, 0ns)

Issues not covered in this section

- Resolution functions
 - Necessary to deal with “write-write-conflicts”
- Inertial delay model
 - Usually, physical gates absorb short pulses
 - Default model
- Transport delay model
 - Transmits all pulses at the inputs ideally

- 1 Overview
- 2 VHDL & FPGAs – rapid prototyping
- 3 First examples
- 4 Testbenches
- 5 Basic syntax
- 6 Data types
- 7 Operators
- 8 Constants, variables & signals
- 9 Entities & architectures
- 10 Components & configurations
- 11 Processes
- 12 Parameterized hardware descriptions
- 13 Semantics
- 14 Evaluation

- Powerful hardware description language
- Hierarchical specifications of concurrent systems
- No nested processes
- No specification of non-functional properties
- No object-orientation
- Static number of processes
- Complicated simulation semantics
- May be too low level for an initial specification of very large digital systems
- Mainly used for hardware generation / synthesis / rapid prototyping (not all VHDL statements are synthesizable!)